



HEATWATCH(Temperature monitoring system)-[Digital and System Designs]

☆ 2 stars

🔗 2 forks

👁 1 watching

🔗

📁

📄 Activity

Branches

Tags

🌐 Public repository

🔗

🔗 1 Branch

📁 0 Tags

🔗

📁

🔍 Go to file

t


Go to file

+

Add file

Code

...

 brcnltk Update README.md	1e5352a · 10 months ago	🕒
📁 LOGISIM	Add files via upload	last year
📁 VERILOG	Add files via upload	last year
📁 VIDEOS	Add files via upload	10 months ago
📄 ABSTRACT-S2-T2 .pdf	Add files via upload	last year
📄 README.md	Update README.md	10 months ago
📄 SNAPSHOT.md	Rename Working.md to SNAPSHOT...	last year

📖 README

✎

☰

HEATWATCH (Temperature monitoring system)

Team

▼ Details

221CS209 - ANSH VIVEK MALHOTRA - anshvivekmalhotra.221cs209@nitk.edu.in

221CS227 - KAKARLA NAVEEN JANAKI RAM - naveenkakarla.221cs227@nitk.edu.in

221CS242 - ROHIT SUNIL - rohitsunil.221cs242@nitk.edu.in

Abstract

▼ Details

The Temperature Monitoring System is a digital project designed to measure and monitor temperature levels in real-time. This system uses digital sensors, microcontrollers, and display units to collect, process, and display temperature data. It can be used in labs after some advancedments. It oCers a practical application for various industries, including environmental monitoring, healthcare, and industrial control. The project involves the integration of a temperature sensor, counter IC, flip-flops, logic gates, a 7-segment LED display,

and power supply components on a breadboard or PCB. It performs various tasks like it records and monitors temperature, it gives a security alarm when Temperature reaches extremes. It displays the Temperature in both Celcius and Fahrenheit. It also displays the average Temperature over 24hrs.

Our motivation is to provide safety measures and safe working conditions for employes. After some advancements we can provide this setup for maintaining optimal Temperature in Industries to make Industrial processes more effecient.



Our unique contribution is Hypothetically we can implement Alarms, maintain optimal temperatureand share data using bluetooth/WiFi



Working

▼ Details

The sensor (Dh t11) measures the atmospheric temperature and sends the value as input directly to a display which is used to display current temperature and it also gives an input to the main circuit after every 30 seconds which is set by using a clock. We use a counter IC to count the number of times we get the temperature inputs.This is an upward counter and it increments every time we get an input from the sensor. The value from the sensor is used as an input to the 11-bit adder in which another 11-bit number is initialized to zero. The result will then be the input for the divider.This result here will be the dividend in this divisor module and the divisor will be the value of the counter. The output from this divisor module is directly displayed using another LCD which is used to display average temperature and the same output is given as an input to 7 flip flops which store each of the 7 bits of the output of divider. Now we are using a 7 by 4 bit multiplier which multiplies the 7-bit ouput from the flip flops and 4 bit output from the counter which is subtracted by 1 using the 4-bit subtractor. The output from this multiplier will be another input for the 11-bit adder which adds the next incoming input to this . The loop goes on and the average temperature is displayed every 30 seconds.

Components-used #Temperature Sensor (e.g., LM35, LM75, or thermistor)

#Counter IC (e.g., 74LS90 or 74LS192).

#Flip-Flops (e.g., 74LS74).

#Logic Gates (e.g., 74LS00, 74LS32).

#Display (e.g., 7-segment LED display).

#Power supply components (voltage regulator, capacitors, etc.).

#Breadboard or PCB for circuit construction.


Logism working

▼ Details

This is our Logism Simulation design.




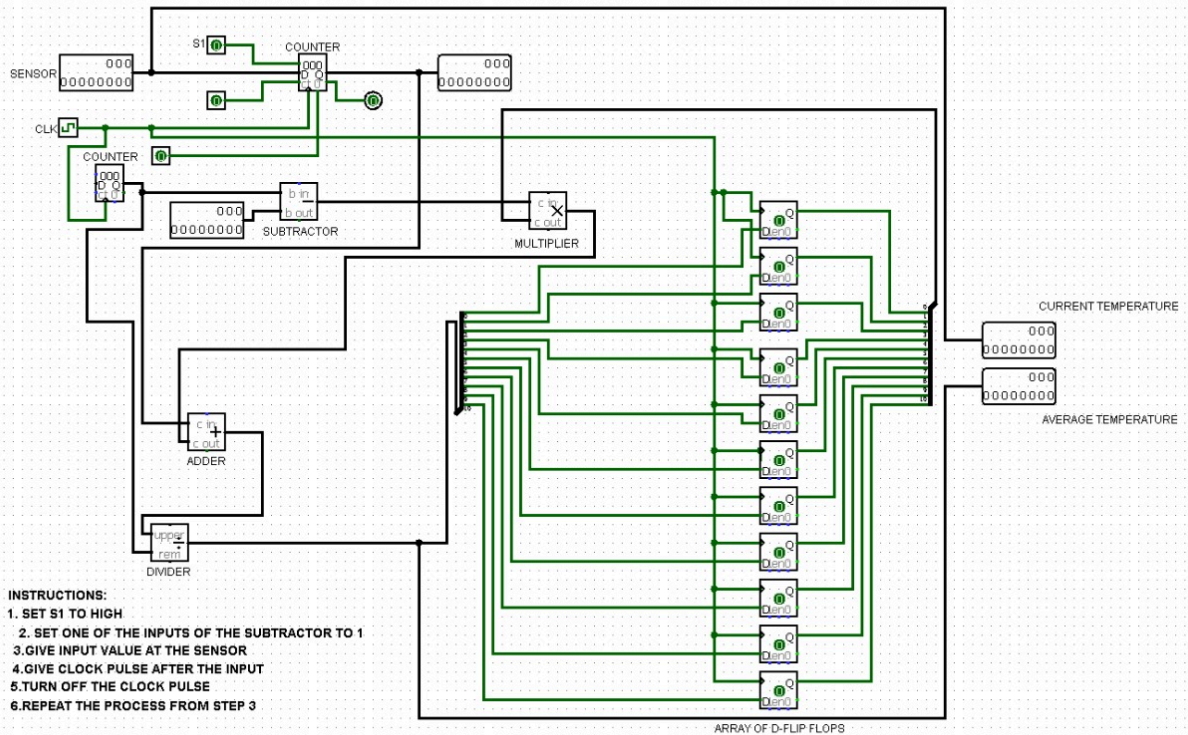
HEAT WATCH:TEMPERATURE MONITORING SYSYTEM



****Iteration 1****-We can see that the input of the numbers through the Temperature sensors is 10 which is 0000001010 in binary, so the current temperature shows the output as 0000001010 and the average output also shows 0000001010 because there is only one single iteration.



▲

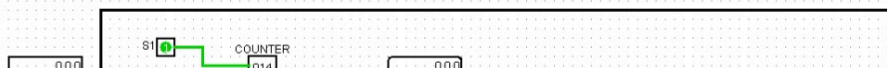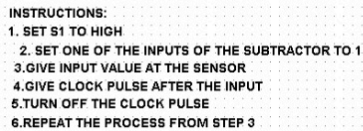

© 2006 The Authors
Journal compilation © 2006 Blackwell Publishing Ltd

No releases published

100

No additional publication





Languages

● Verilog 100.0%